

IITB CPU

November 30, 2022

Abhishek Savaliya	21D070065
Simran Singh	21D070073
Jangid Nikita	21D070032
Lohitaksh Mahajan	21D070042

Contents

1	Overview of the Design	2
2	Working of Design	2
3	Component Memory	3
4	Component Register	3
5	Final Design	5
6	Running Instructions	6
7	Generating Fibonacci Sequence	7

1 Overview of the Design

We started our design by first writing the states for every instruction without considering state minimization. After then we started to minimize the states. After effective minimization we had a total of 33 states with state 1 and 2 common to all. To minimize states we used different muxes(if else conditions). After state minimization we constructed individual components and then made pen paper design of our data path. Below is the diagram of our data path:

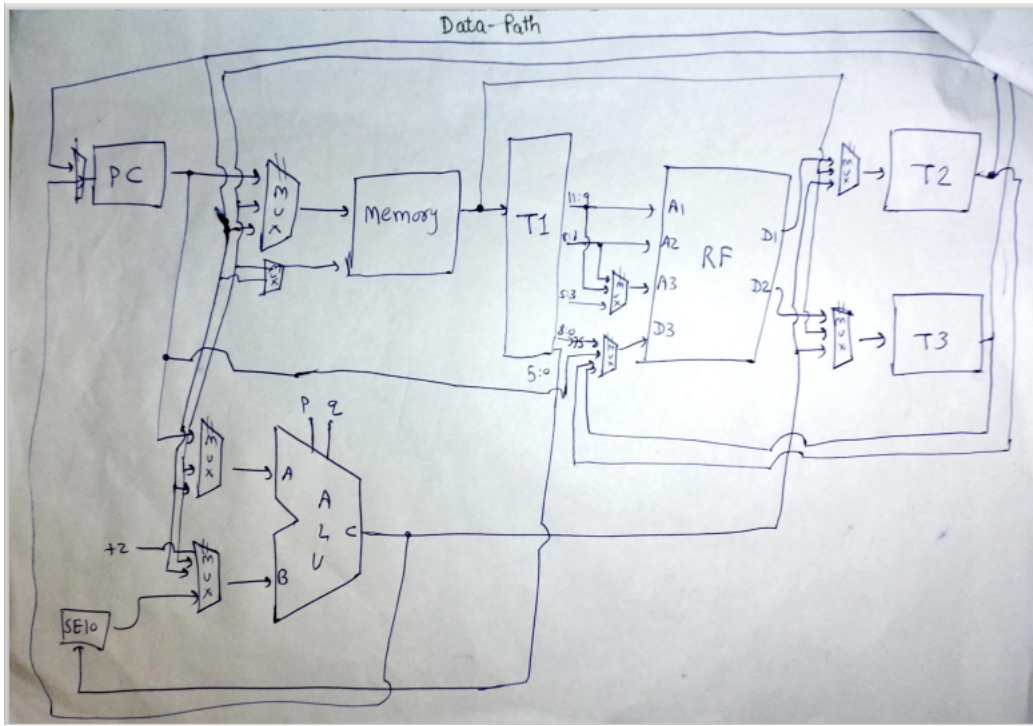


Figure 1: Pen Paper Design of Data Path

2 Working of Design

Our CPU works by moving the program counter 1 step ahead after every instruction. To stop the instructions we added an extra state *111111* which is an infinite state i.e. if it comes, it remains forever. Memory contains all the instructions and all the data to be fed into registers. Registers are

16 bit storage devices. We constructed 8 registers from R0 to R7. A FSM was made to guide the CPU through particular states. In each particular state; our ALU, PC, Memory and Temporary Registers had particular tasks to perform.

3 Component Memory

IITB-CPU is a 16-bit microprocessor having 64 bytes of data memory and 64 bytes of instruction memory. Instructions can be given to the processor using the memory.vhdl file in which the instructions can be directly fed into the instruction memory array.

```

18
19 architecture working of mem is
20 type mem_array is array (0 to 31) of std_logic_vector (15 downto 0);
21 signal mem_data: mem_array :=(
22   x"0000",x"0000", x"0000", x"0000",
23   x"0000",x"0000", x"0000", x"0000",
24   x"0000",x"0000", x"0000", x"0000",
25   x"0000",x"0000", x"0000", x"0000",
26   x"0000",x"0000", x"0000", x"0000",
27   x"0000",x"0000", x"0000", x"0000",
28   x"0000",x"0000", x"0000", x"0000",
29   x"0000",x"0000", x"0000", x"0000"
30 );
31
32
33 signal mem_ins: mem_array := (
34   b"0000000001010000",x"FFFF", x"FFFF", x"FFFF",
35   x"FFFF",x"FFFF", x"FFFF", x"0000",
36   x"0000",x"0000", x"0000", x"0000",
37   x"0000",x"0000", x"0000", x"0000",
38   x"0000",x"0000", x"0000", x"0000",
39   x"0000",x"0000", x"0000", x"0000",
40   x"0000",x"0000", x"0000", x"0000",
41   x"0000",x"0000", x"0000", x"0000"
42 );
43 begin
44 mem_action: process(clk)
45 begin
46 if (rising_edge(clk)) then
47 if (state="001011" and op_code= "0101") then ---s11 for sw
48   mem_data(to_integer(unsigned(t3_addr))) <= data_t2;
49 elsif (state="001011" and op_code= "0111") then ---s11 for sm
50   mem_data(to_integer(unsigned(t2_addr))) <= data_t3;
51 end if;
52 end if;
53 end process;

```

Figure 2: Component Memory

4 Component Register

We constructed 8 registers R0 to R7 each being 16 bit storage device. Registers can be accessed through register.vhdl file. Below image shows value 1

stored in register 0 and 1. R7 contains our PC.

```

7  entity registers is
8  | port (reg_a1: in std_logic_vector(2 downto 0);
9  |       reg_a2: in std_logic_vector(2 downto 0);
10 |       reg_a3: in std_logic_vector(2 downto 0);
11 |       t2: out std_logic_vector(15 downto 0);
12 |       t2_in: in std_logic_vector(15 downto 0);
13 |       t3: out std_logic_vector(15 downto 0);
14 |       t3_in: in std_logic_vector(15 downto 0);
15 |       shift7: in std_logic_vector(15 downto 0);
16 |       clk: in std_logic;
17 |       state: in std_logic_vector(5 downto 0);
18 |       pc: in std_logic_vector(15 downto 0);
19 |       pc_update: in std_logic_vector(15 downto 0)
20 | );
21  end entity;
22
23  architecture working of registers is
24  | type mem_array is array (0 to 7 ) of std_logic_vector (15 downto 0);
25  | signal regs: mem_array :=(
26  |   x"0001",x"0001", x"0000", x"FFFF",
27  |   x"FFFF",x"FFFF", x"FFFF", x"FFFF"
28  | );
29  begin
30  | regs_read: process(reg_a1, reg_a2, state)
31  | begin
32  |   if (state = "000010") then
33  |       t2 <= regs(to_integer(unsigned(reg_a1)));
34  |       t3 <= regs(to_integer(unsigned(reg_a2)));
35  |   elsif (state="011010") then
36  |       t3 <= regs(0);
37  |   elsif (state="011011") then
38  |       t3 <= regs(1);
39  |   elsif (state="011100") then
40  |       t3 <= regs(2);
41  |   elsif (state="011101") then
42  |       t3 <= regs(3);
43  |   elsif (state="011110") then
44  |       t3 <= regs(4);

```

Figure 3: Component Register

5 Final Design

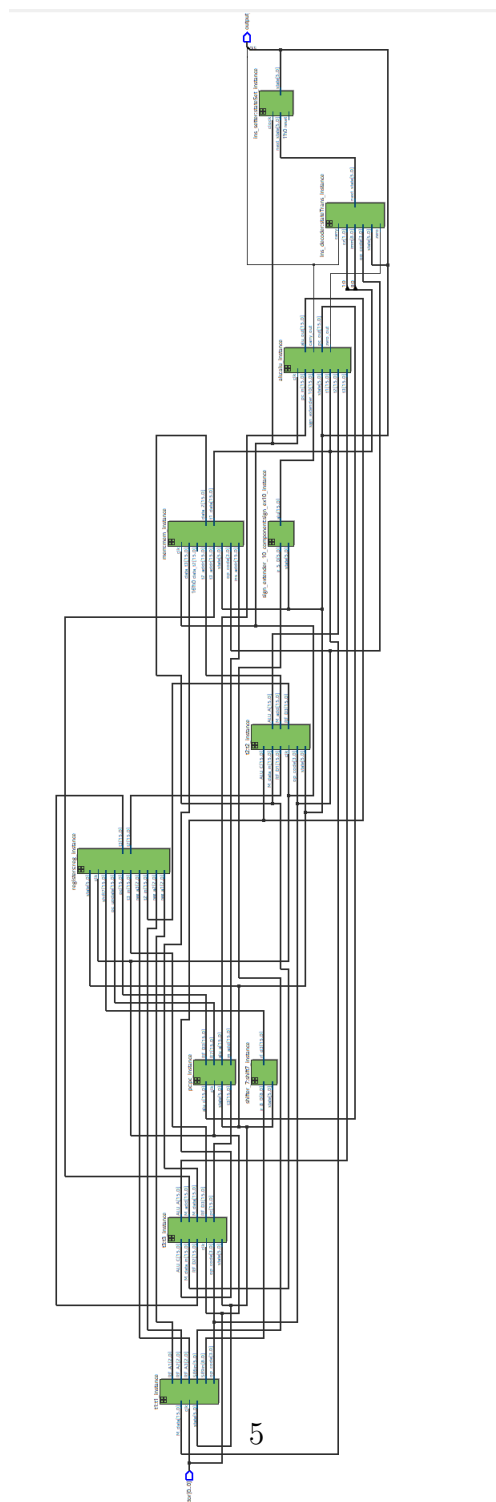


Figure 4: Netlist View

6 Running Instructions

Below images shows the add instruction in our CPU. State transition flows from S1 to S4 and the input of Register 0 and Register 1 being stored in Register 2. PC updates by 1 step.



Figure 5: RTL Wave

 


Figure 6: Register Data

7 Generating Fibonacci Sequence

Below is just a fun demo code run by our CPU. We generated a fibonacci sequence in our registers by giving following instructions as input.

```
signal mem_ins: mem_array := (
b"0000000001010000",b"0000001010011000", b"0000010011100000", b"000001100101000",
b"0000100101110000",b"0000101110111000", x"FFFF", x"0000",
x"0000",x"0000", x"0000", x"0000",
x"0000",x"0000", x"0000", x"0000",
x"0000",x"0000", x"0000", x"0000",
x"0000",x"0000", x"0000", x"0000",
x"0000",x"0000", x"0000", x"0000",
x"0000",x"0000", x"0000", x"0000",
x"0000",x"0000", x"0000", x"0000",
x"0000",x"0000", x"0000", x"0000",
);
```

Figure 7: Fibonacci Input

 


Figure 8: Fibonacci Sequence